

# Analog VLSI Circuits

## Lab 4

September 2024

### PART1: SIMPLE CURRENT MIRROR DESIGN

Explore current mirror using nmos transistor cells from the gpdk180 library.

 


Figure 1: Simple NMOS current mirror

- Design a current mirror for input reference current of  $I_i = 10 \mu\text{A}$  and output current of  $I_o = 30 \mu\text{A}$  (initial design 1) Sweep  $V_{out}$  and plot % error  $((I_{o,sim} - I_o) \times 100 / I_o)$  as a function of  $V_{out}$ .
- How can you reduce error in a)? (Hint: increase L, why?). Sweep L and plot change in error with increasing L for a fixed  $V_{out}$  (for example  $V_{out} = V_{DD}$ ).
- Use initial design, sweep temperature from -40 to 150 C and plot the effect on % error. Can you reduce error by increasing  $V_{od}$  (Hint: decrease W/L)? For this question, plot a family of curve with % error vs. temperature for different  $V_{od}$ .
- Based on the results of a), b) and c) finalize a design (final design 1) of the current mirror i.e., W/L values for M1 and M2 and provide your justification.
- Repeat the exercise for smaller current  $I_i = 100 \text{ nA}$ , and  $I_o = 3 \mu\text{A}$ , i.e., start with initial design 2 and follow the procedure above to obtain final design 2. Note that you would require large L to satisfy sufficient  $V_{od}$ . Compare the estimated area of final design 1 and final design 2.
- Use the final designs 1 and 2 and provide a step in the respective input current  $I_i$  with rise time of 100 ps. Plot the transient settling of  $I_o$  with time. Calculate the 10% to 90% rise times. Comment on the results.
- Draw the layout of the final design 1. Write and justify the layout considerations you made.

## PART2: SELF-BIASED HIGH SWING CURRENT MIRROR DESIGN

Design a high-swing current mirror using pmos transistor cells from the gpdk180 library with  $I_{ref} = 10\mu A$  and  $I_{out} = 50\mu A$ . Use  $V_{od} = 200mV$  for the mirror device  $M_1$  and  $M_2$ . Use  $V_{od} = 50mV$  for the cascode devices  $M_3$  and  $M_4$ .

 


Figure 2: High swing PMOS current mirror

Characterize the following:

- Perform a DC operating point simulation with  $V_{out} = V_{DD}/2$  at room temperature. Annotate the DC operating voltages. Calculate output impedance  $R_{out}$  from the DC operating point of the devices. Calculate the minimum required output voltage ( $V_{out,min}$ ).
- Output current vs. output voltage using a DC sweep of  $V_{out}$ . Plot  $I_{out}$  vs  $V_{out}$ . Calculate  $R_{out}$  from the  $I_{out}$  vs.  $V_{out}$  curve. Plot % error with respect to the ideal output vs.  $V_{out}$ . From the error plot estimate the operating output voltage range. Compare the result with a).
- Characterize output impedance  $R_{out}$  for  $V_{out} = V_{DD}/2$  using AC simulation. Compare with a) and b).
- Perform a temperature sweep from -50C to 150C for  $V_{out} = V_{DD}/2$  and plot % error vs. temperatur